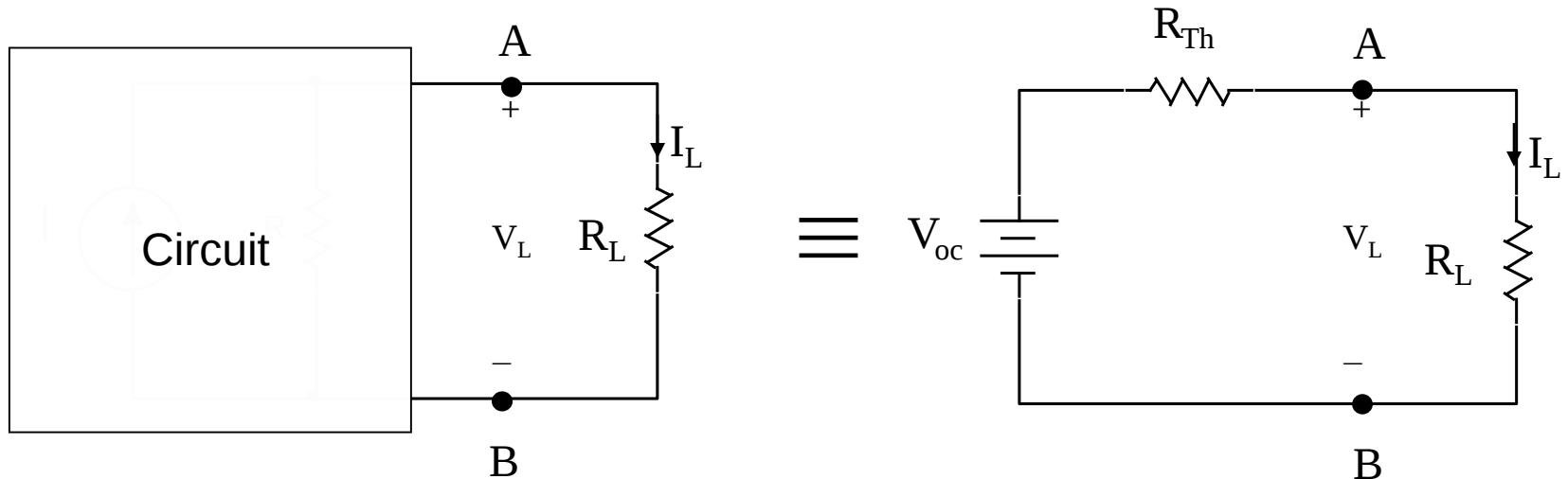


Electric Circuits I
ELEC 305

Thevenin's and Norton's
Theorems

Thevenin's Theorem



V_{oc} : Open-circuit voltage between terminals A & B

R_{Th} : Equivalent resistance between terminals A & B with all independent sources are killed

Applying Thevenin's Theorem

- Remove the load (open the circuit between the load terminals)
- Find V_{oc} by applying all known circuit analysis techniques
- Determine the equivalent resistance of the circuit at the terminals (R_{Th})
- Connect the load to V_{oc} and R_{Th} to the load terminals and determine the required current or voltage .

Thevenin's Equivalent Resistance

The calculation of R_{Th} depends on the type of sources in the circuit as follows:

1- Independent Sources only:

voltage and current sources are killed and the equivalent resistance is calculated

2- Dependent Sources only:

an external independent voltage /current source is applied at the open terminals and the corresponding current/voltage is determined. The voltage/current ratio is Thevenin's resistance (R_{Th})

Thevenin's Equivalent Resistance

3- Both Independent and Dependent Sources:


The open terminals are shorted and the short-circuit current is determined. The ratio of the open-circuit voltage to the short-circuit current is Thevenin's resistance (R_{Th})

1- Circuits Containing Only Independent Sources

Example #1

Find the voltage V_o using


(a) Thevenin's theorem

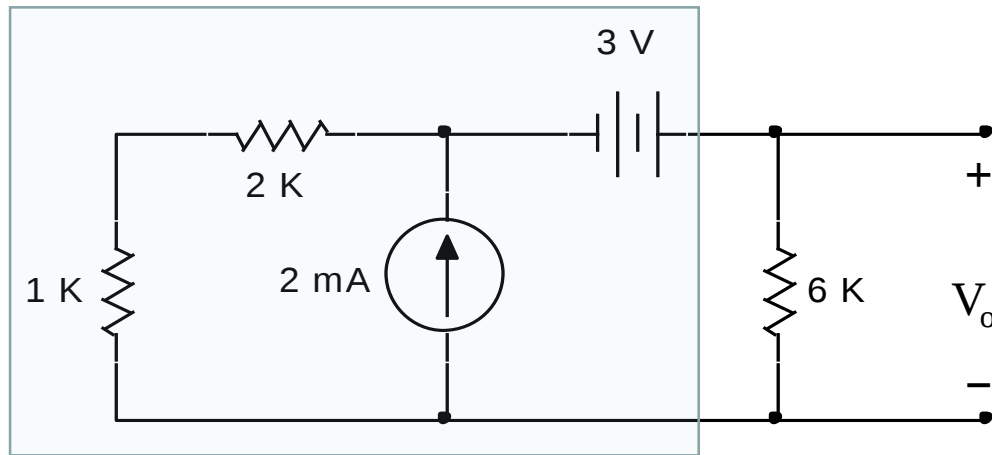

Solution using Thevenin's Theorem

1- Open the circuit at the load terminals

2- Calculate V_{oc}

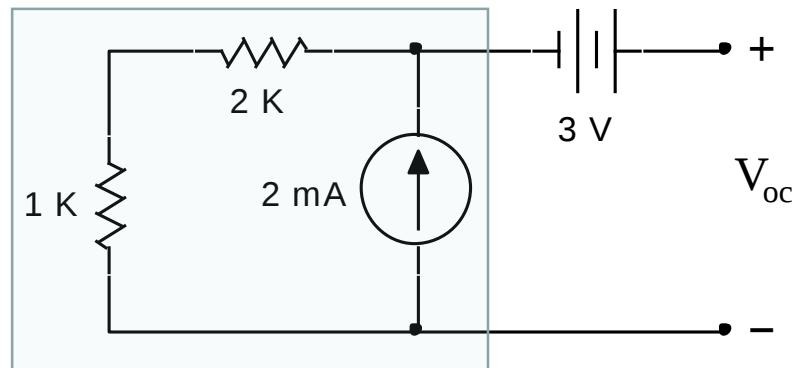

Using source transformation, we get a 6 V source


6 V source in series with a resistor and the 3 V source →

$$V_{oc} = 3 + 6 = 9\text{ V}$$

Solution using Thevenin's Theorem

3- Determine R_{Th} :

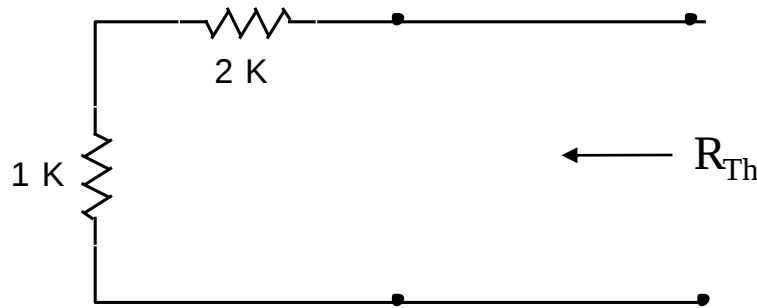- Short-circuit the voltage sources and open-circuit the current source →




- Calculate the equivalent resistance

$$R_{Th} = 2\text{ K} + 1\text{ K} = 3\text{ K}$$

Solution using Thevenin's Theorem

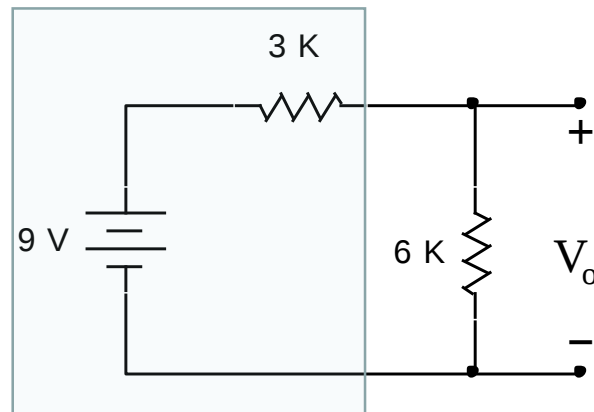4- Connect the load to Thevenin's equivalent circuit, and calculate V_o




Using voltage division rule:

$$V_o = 9 \times 6 / (6 + 3) = 6 \text{ V}$$

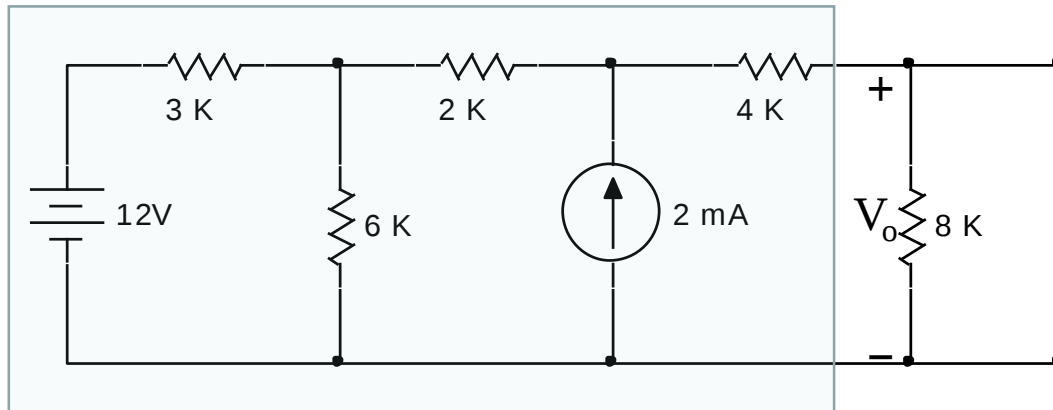
Example #2

Find the voltage V_o using Thevenin's theorem.



- 1- Open the circuit at the load terminals
- 2- Calculate V_{oc}

Solution

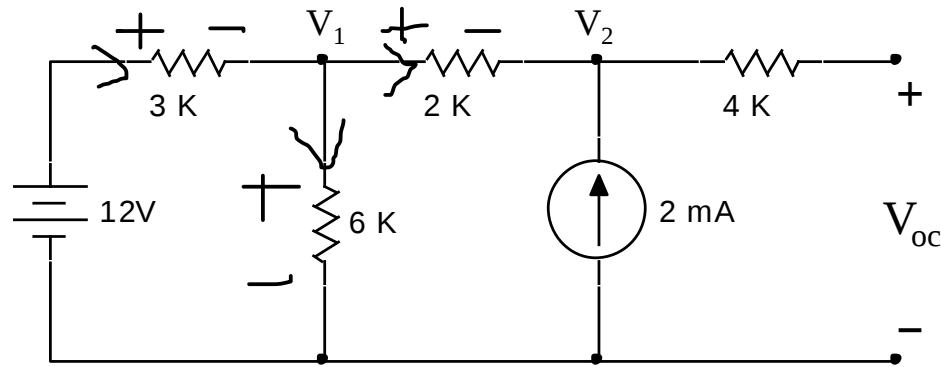

Using nodal analysis:

$$(12 - V_1) / 3 - V_1 / 6 - (V_1 - V_2) / 2 = 0 \quad (1)$$

$$(V_1 - V_2) / 2 + 2 = 0 \quad (2)$$


Solving the equations simultaneously yields:

$$V_2 = 16 \rightarrow V_{oc} = 16$$

Solution

3- Determine R_{Th} :

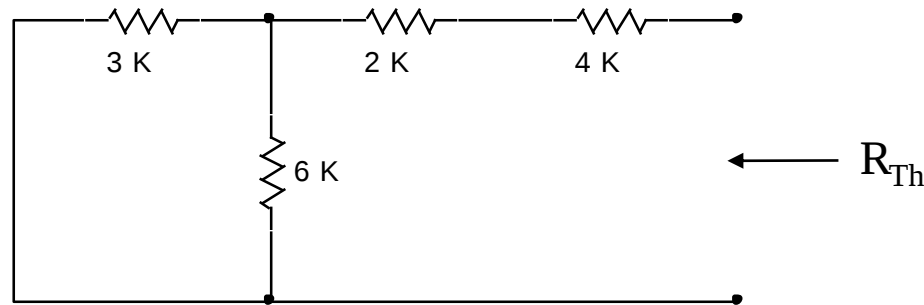- Short-circuit the voltage sources and open-circuit the current source →




- Calculate the equivalent resistance

$$R_{Th} = 2\text{ K} + 4\text{ K} + (6\text{ K} // 3\text{ K}) = 8\text{ K}$$

Solution

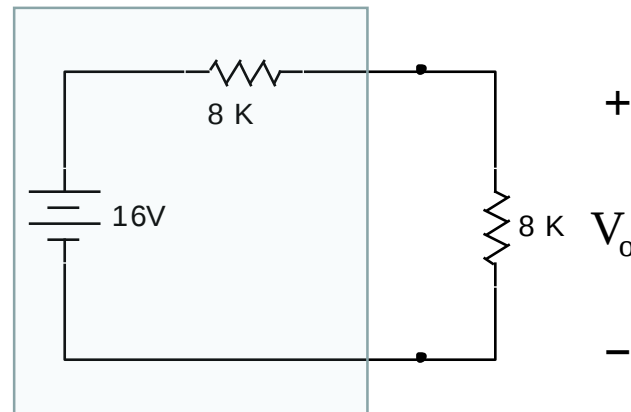4- Connect the load to Thevenin's equivalent circuit, and calculate V_o




Using simple voltage division:

$$V_o = 16 / 2 = 8 \text{ V}$$

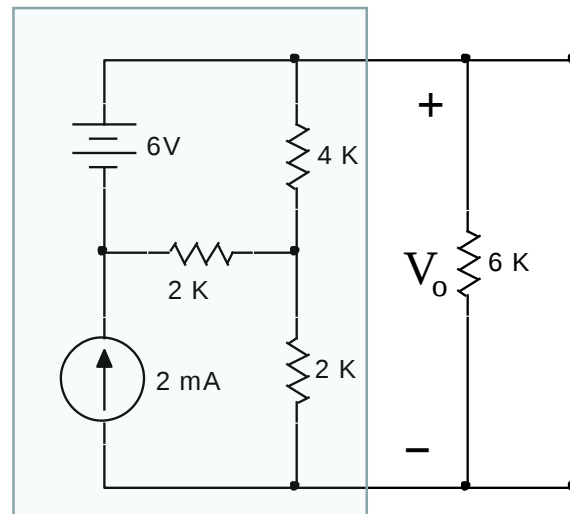Example #3

Find the voltage V_o using Thevenin's theorem



1- Open the circuit at the load terminals

2- Calculate V_{oc}

Solution

Using loop analysis:


$$I_2 = 2 \text{ mA}$$

$$4 I_1 + 2(I_1 - I_2) - 6 = 0$$

→

$$I_1 = 5/3 \text{ mA}$$

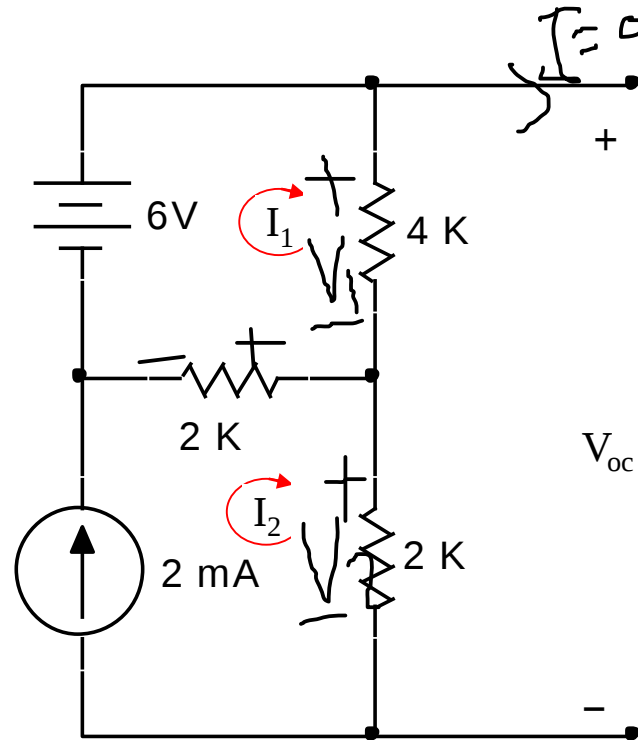
$$\begin{aligned} V_{oc} &= 4 I_1 + 2 I_2 \\ &= 4 * 5/3 + 2 * 2 = 32/3 \end{aligned}$$



Solution

3- Determine R_{Th} :

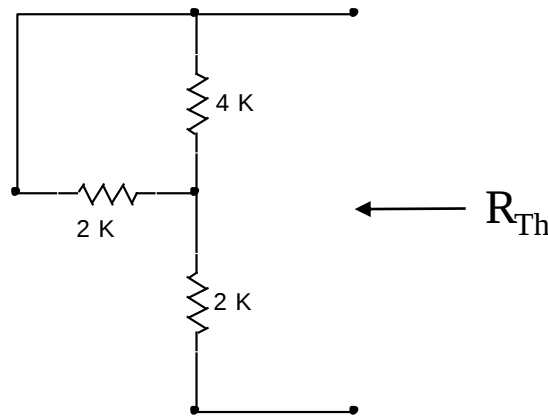- Short-circuit the voltage sources and open-circuit the current source →




- Calculate the equivalent resistance

$$R_{Th} = 2 \text{ K} + (4 \text{ K} // 2 \text{ K}) = 10/3 \text{ K}$$

Solution

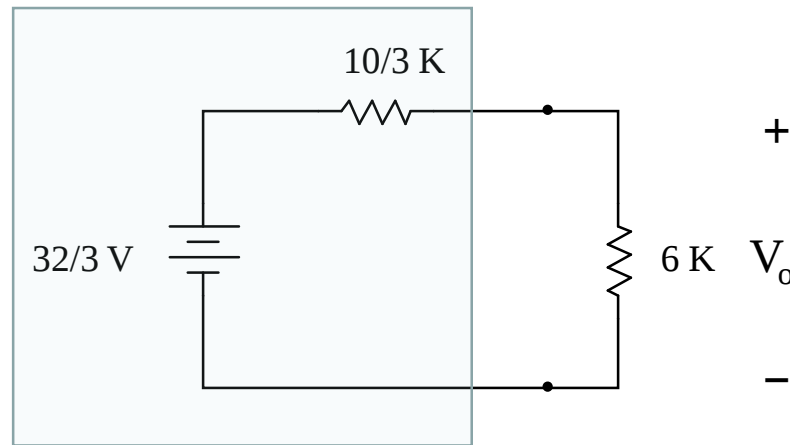4- Connect the load to Thevenin's equivalent circuit, and calculate V_o




Using voltage division rule:

$$V_o = (32/2) * 6 / (6 + 10/3) = 48/7 \text{ V}$$

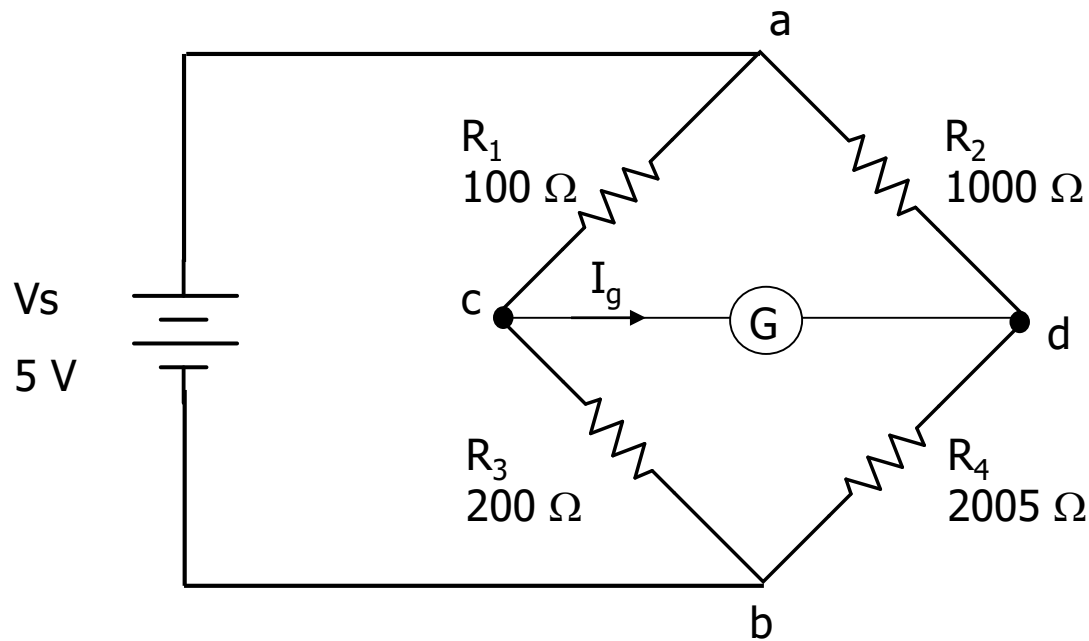Example #4: Wheatstone Bridge

Calculate the current I_g , if the resistance of the galvanometer is $100\ \Omega$.




Solution


- Open the circuit between terminals 'c' and 'd', and find the equivalent voltage and equivalent resistance

- Thevenin's equivalent voltage V_{oc} :
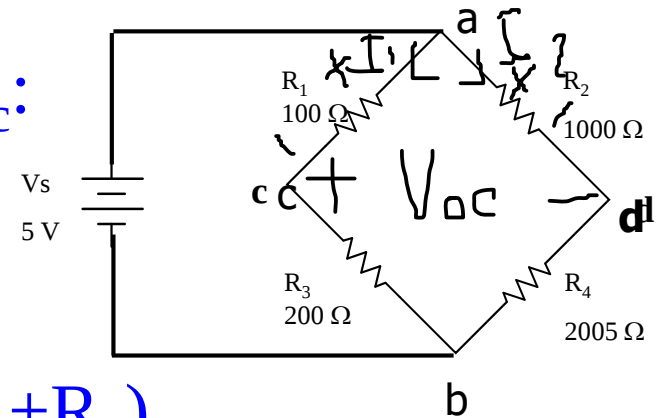
$$\begin{aligned} V_{oc} &= V_{cb} - V_{db} \\ &= I_1 R_3 - I_2 R_4 \\ &= V_s R_3 / (R_1 + R_3) - V_s R_4 / (R_2 + R_4) \\ &= 5 (200/300 - 2005/3005) \\ &= -2.77 \text{ mV} \end{aligned}$$




Solution

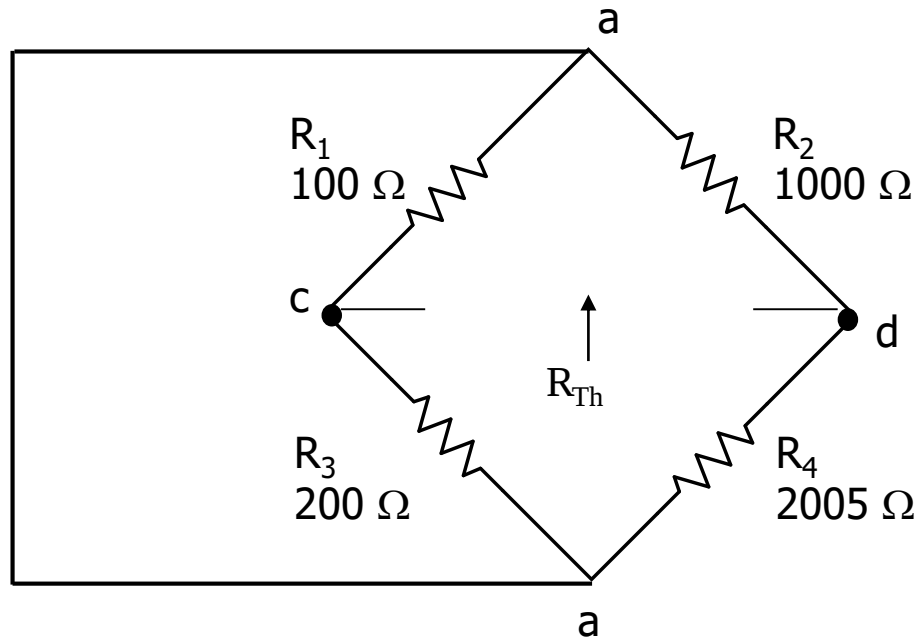

$$\begin{aligned} R_{Th} &= R_1 // R_3 + R_2 // R_4 \\ &= 100 // 200 + 1000 // 2005 = 734\ \Omega \end{aligned}$$

Solution

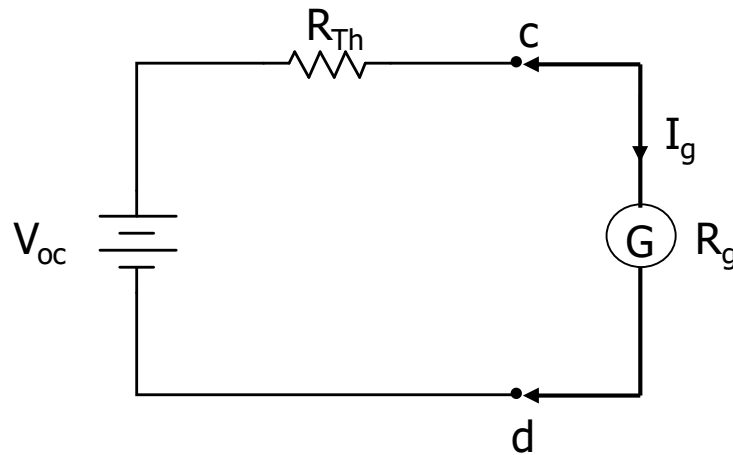


When the galvanometer is connected to the output terminals of the Thevenin's equivalent circuit:


$$\begin{aligned} I_g &= V_{oc} / (R_{Th} + R_g) \\ &= -2.77 \text{ mV} / (734 + 100) = -3.4 \text{ } \mu\text{A} \end{aligned}$$

Example #5

Use Thevenin's theorem to find I_o

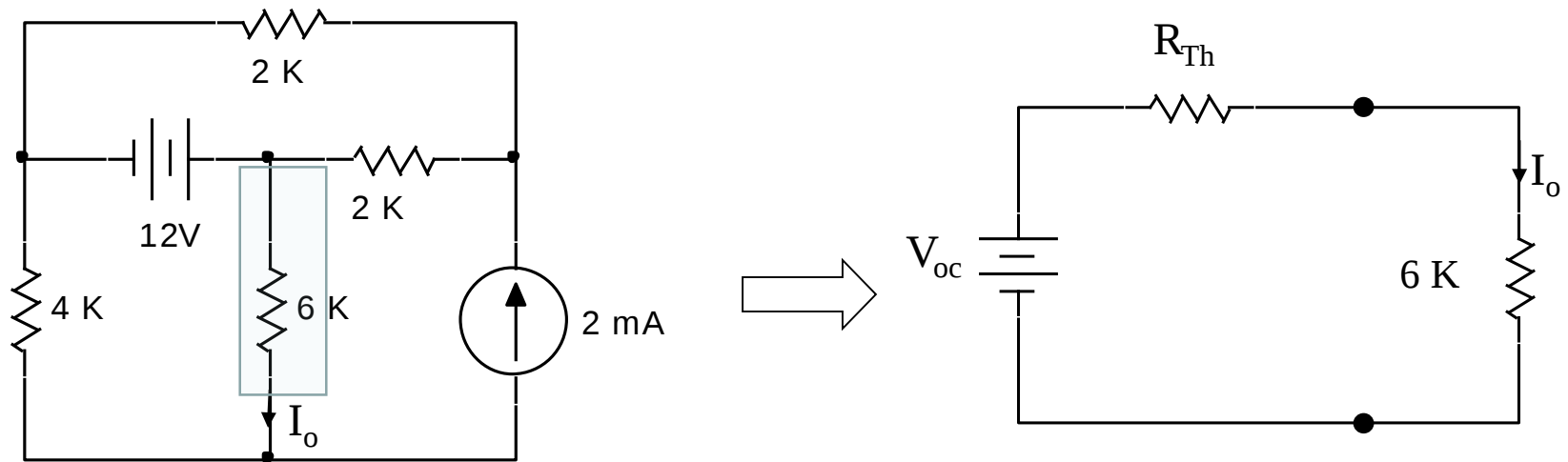


Solution

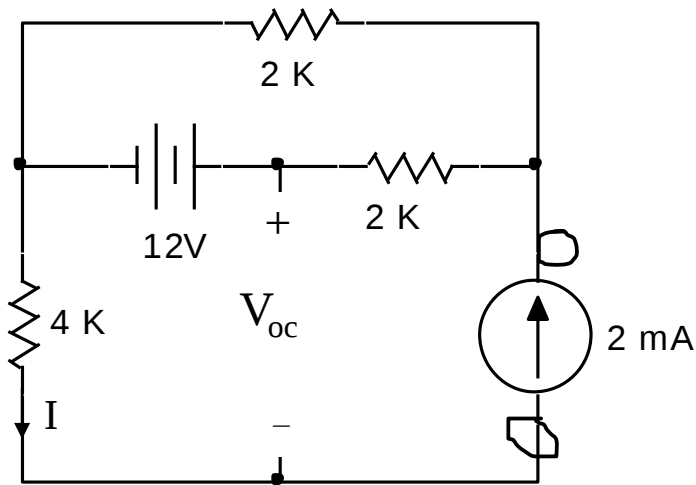

$$I = 2 \text{ mA}$$

$$V_{oc} = 12 + 4 * I$$


$$= 12 + 4 * 2 = 20 \text{ V}$$

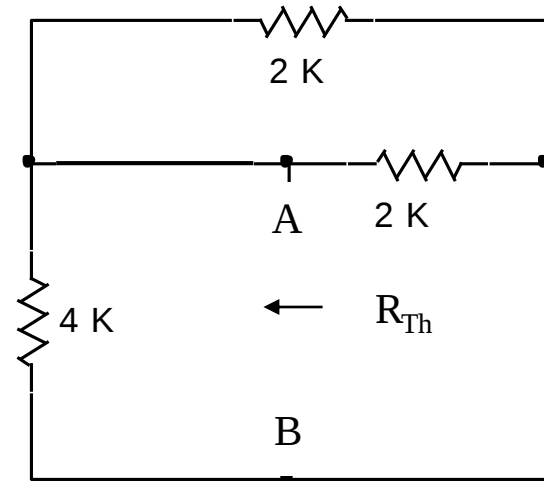

Since the $(2K+2K)$ is in parallel with a short circuit:

$$R_{Th} = R_{AB} = 4 \text{ K}$$

Solution

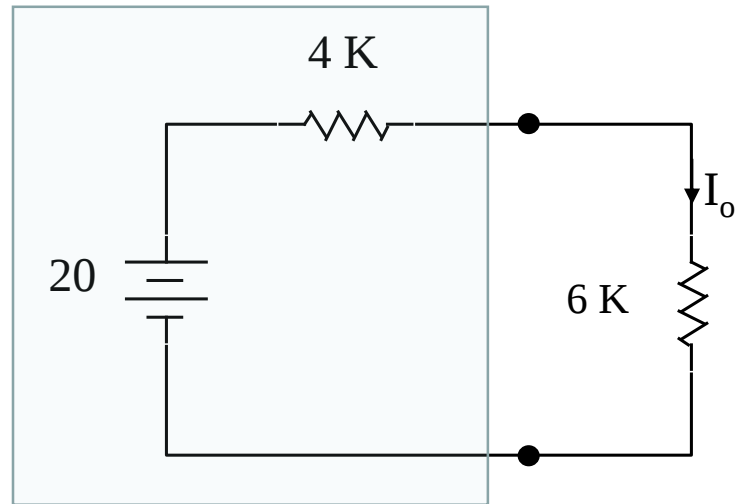

Connecting the load to Thevenin's equivalent circuit

$$\begin{aligned}\rightarrow I_o &= 20 / (4+6)\text{K} \\ &= 20 / 10 \text{ K} = 2 \text{ mA}\end{aligned}$$


Circuits Containing Only Dependent Sources

Circuits containing only dependent sources


- In this case:
 - $V_{oc} = 0$
 - $I_{sc} = 0$
- Thevenin's / Norton's equivalent circuit consists of R_{Th} only
- To calculate R_{Th} , an independent voltage /current source is applied at the open terminals and the corresponding current/voltage is determined. The ratio between voltage and current is Thevenin's resistance (R_{Th})

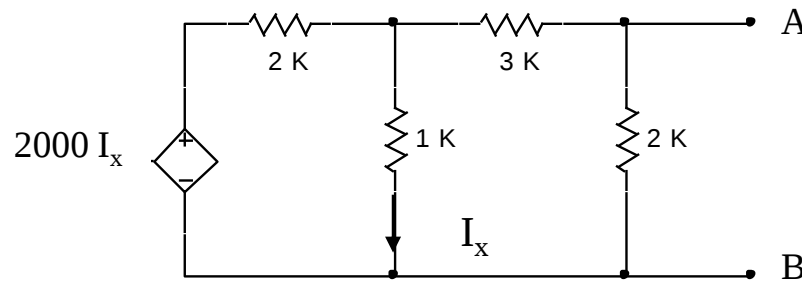Example #8

Determine Thevenin's equivalent circuit at terminals A-B.




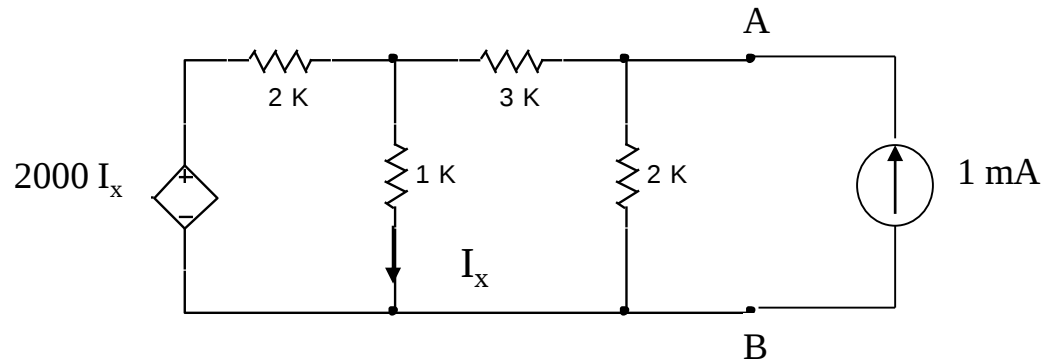Solution: 1- Apply a current source at the terminals



Solution

2- Determine V_{AB}

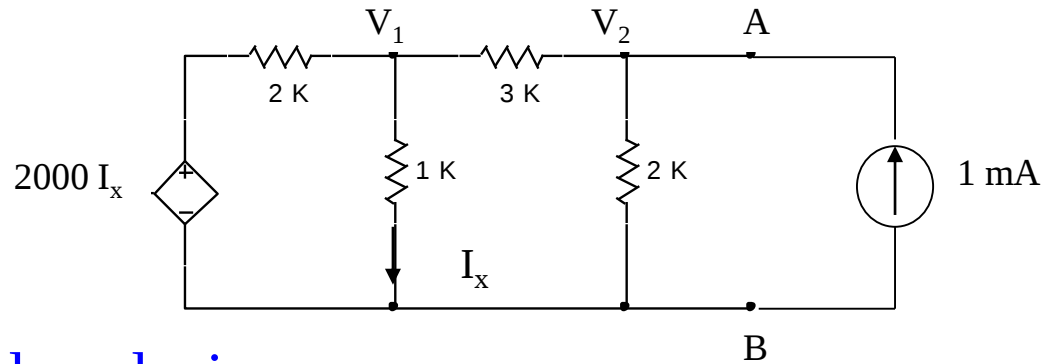

Using nodal analysis:

$$(2 I_x - V_1)/2 - V_1/1 - (V_1 - V_2)/3 = 0 \quad (1)$$

$$(V_1 - V_2)/3 - V_2/2 + 1 = 0 \quad (2)$$

Also,

$$I_x = V_1/1 \quad (3)$$

Solution

Solving the equations simultaneously yields:

$$V_2 = 10/7$$





$$V_{AB} = 10/7$$

3- Determine R_{Th}

$$\begin{aligned} R_{Th} &= V_{AB} / (\text{applied current}) \\ &= V_{AB} / 1 \text{ mA} \\ &= 10/7 \text{ K} \end{aligned}$$

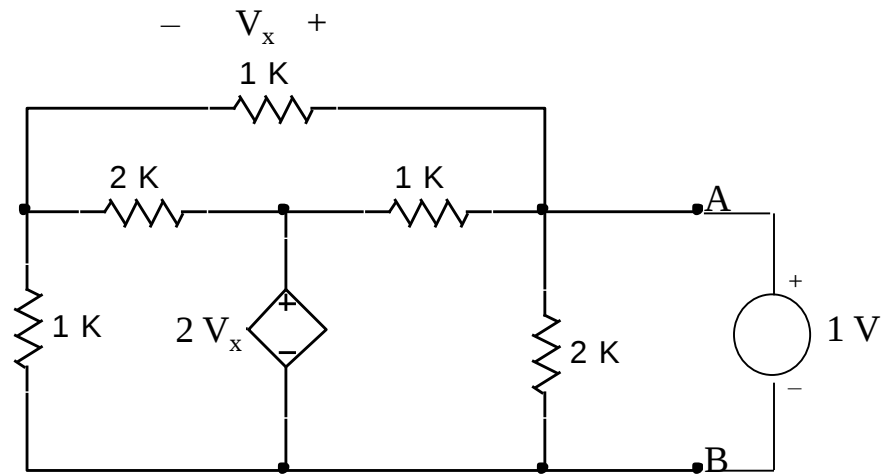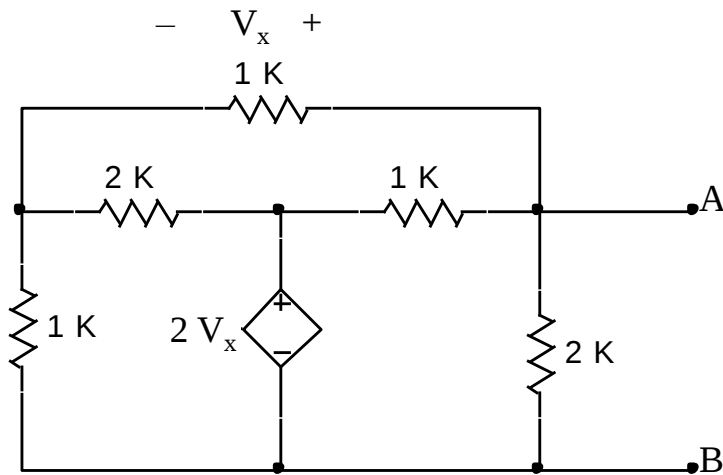Example #9


Determine Thevenin's equivalent circuit at terminals A-B.



Solution: 1- Apply a voltage source at the terminals

Solution

2- Determine I_o

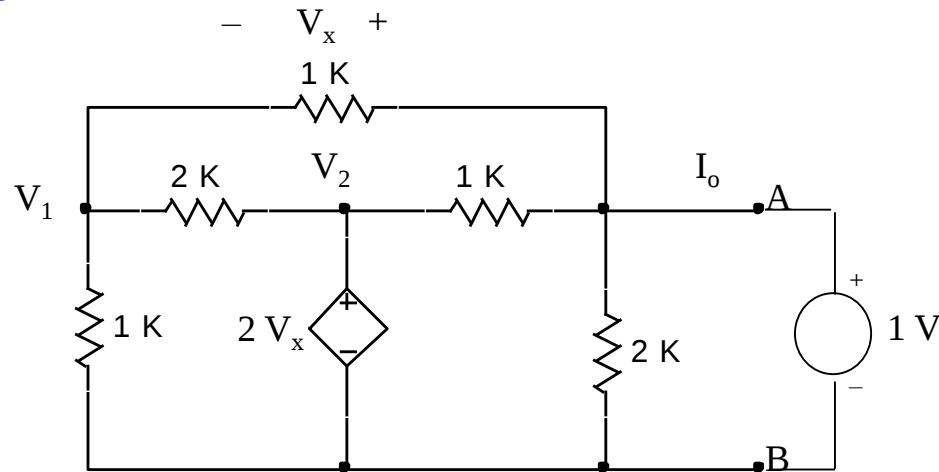

Using nodal analysis:

$$V_1/1 + (V_1 - V_2)/2 + (V_1 - 1)/1 = 0 \quad (1)$$

$$V_2 = 2 V_x \quad (2)$$

Solution

Also,

$$1 - V_1 = V_x$$

Solving the equations simultaneously yields:

$$V_x = 3/7 \text{ V}$$

Hence the current I_o :

$$I_o = 1/2\text{K} + V_x/1\text{K} + (1 - 2V_x)/1\text{K} = 15/14 \text{ mA}$$

Finally,

$$R_{Th} = 1\text{V} / I_o = 14/15 \text{ K}$$

Circuits Containing Both Independent and Dependent Sources

Circuits containing both independent and dependent sources

- In this case, both the open-circuit voltage (V_{oc}) and the short-circuit current (I_{sc}) are determined
- The equivalent resistance (R_{Th}) is calculated as:

$$R_{Th} = V_{oc} / I_{sc}$$

Use Thevenin's theorem to find V_o

Solution: First find V_{oc} using loop analysis:

$$I_2 = 2 \text{ mA}$$


$$I_1 = V_x / 2 \text{ mA}$$

$$V_x = 4 (I_1 - I_2)$$

$$I_1 = 4 (I_1 - I_2) / 2$$

$$\rightarrow I_1 = 4 \text{ mA}$$

$$V_{oc} = 3 + 2 I_1 = 11 \text{ V}$$

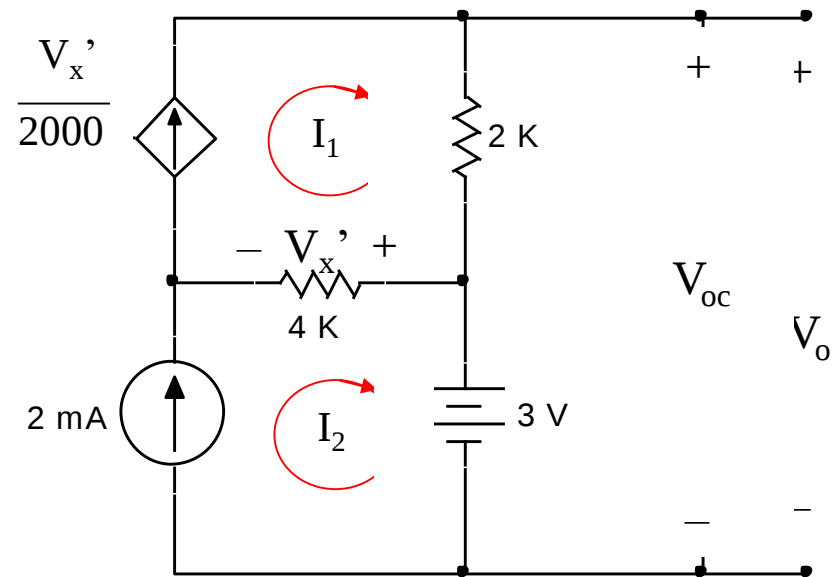

Solution


Determine I_{sc} using nodal analysis, assuming the reference node as indicated in the circuit diagram.

At node 1:

$$2 + V_x''/4 - V_x''/2 = 0$$

$$V_x'' = 8 \text{ V}$$

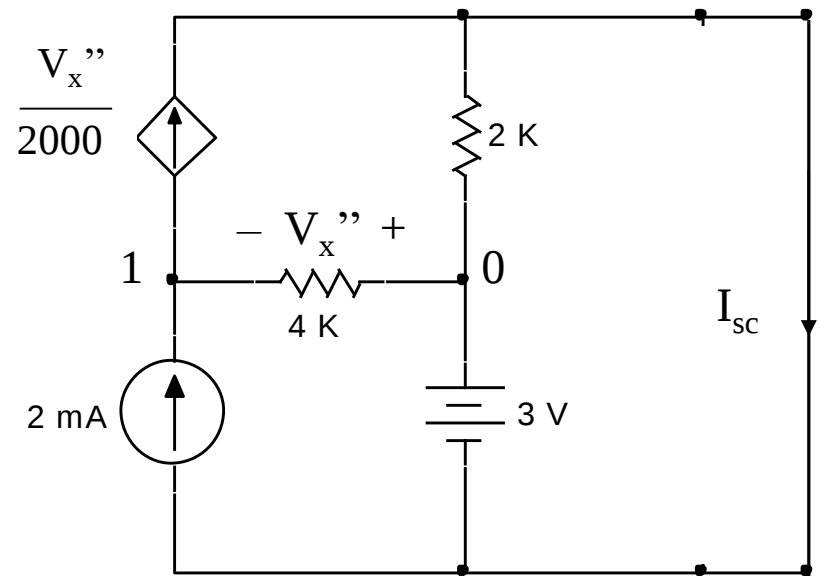
$$\begin{aligned} I_{sc} &= I_{2K} + V_x''/2 \\ &= 3/2 + 8/2 \\ &= 11/2 \text{ mA} \end{aligned}$$



Solution

$$R_{Th} = V_{oc} / I_{sc} = 11 / (11/2) = 2 \text{ K}$$

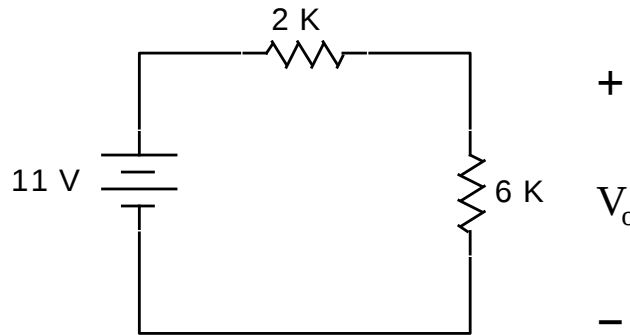
Connect Thevenin's equivalent circuit to the remainder of the network, and determine V_o :



$$\begin{aligned} V_o &= 11 \cdot 6 / (6+2) \\ &= 33/4 \text{ V} \end{aligned}$$


Example #11

Use Thevenin's theorem to find V_o

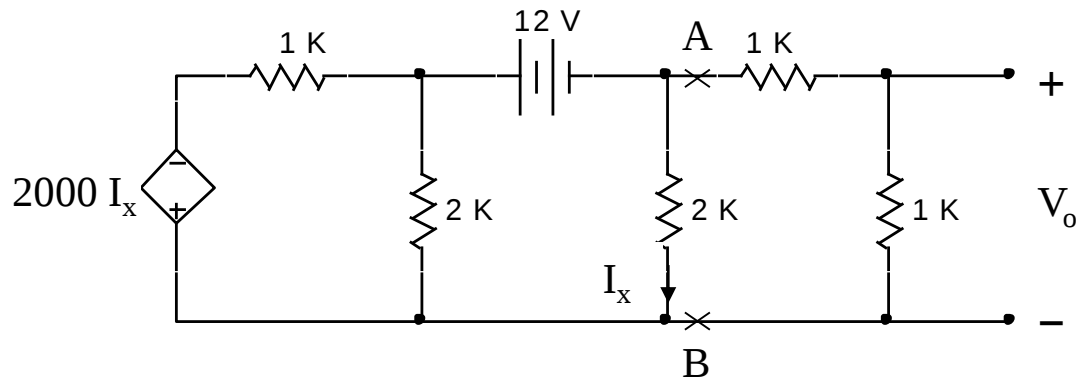

Solution: Open the circuit at terminals A-B, and find
Thevenin's equivalent circuit between these terminals

Solution

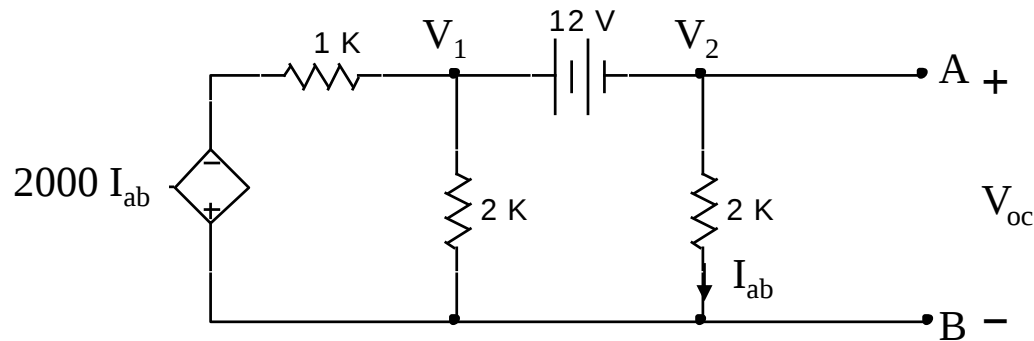

Use nodal analysis to determine V_{oc} :


$$V_1 - V_2 = 12 \quad (1)$$

$$(V_1 - (-2I_{ab}))/1 + V_1/2 + V_2/2 \quad (2)$$

$$I_{ab} = V_2/2 \quad (3)$$

Solving the equations simultaneously yields: $V_2 = -6\text{ V}$

Solution

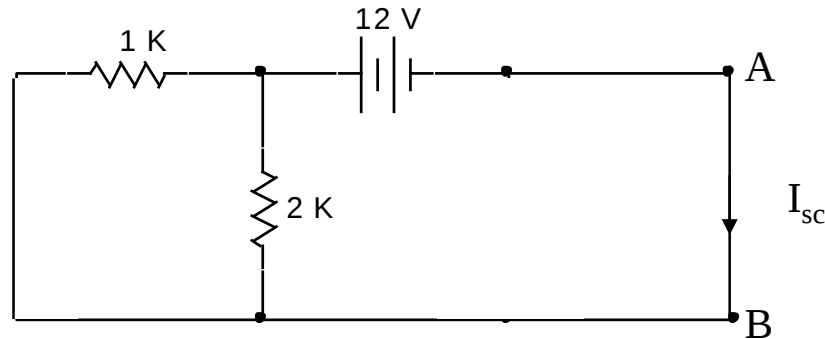


Short circuit $\rightarrow I_{ab} = 0 \rightarrow 2000 I_{ab} = 0$

Determine I_{sc} :

$$I_{sc} = -12 / (1 // 2) = -12 / (2/3) = -18 \text{ mA}$$

$$R_{Th} = V_{oc} / I_{sc} = (-6) / (-18) = 1/3 \text{ K}$$


Solution

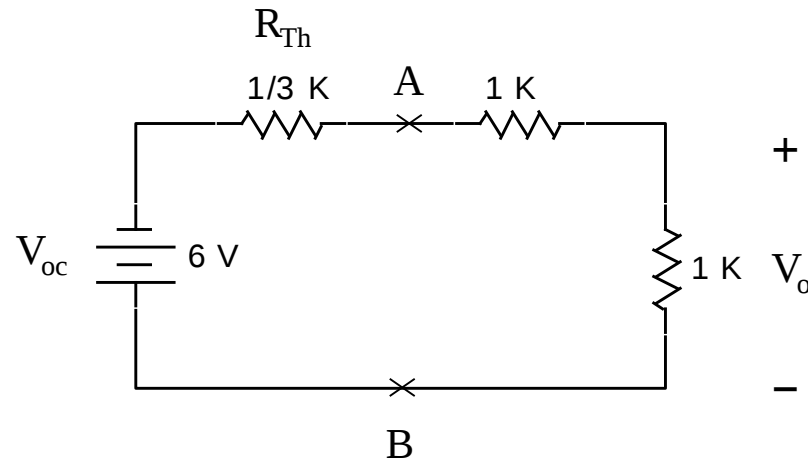

Connect Thevenin's equivalent circuit to the remainder of the network at terminals A-B, and determine V_o :

$$\begin{aligned} V_o &= -6 * 1 / (1 + 1 + (1/3)) \\ &= -6 / (7/3) = -2.57\text{ V} \end{aligned}$$


Norton's Theorem

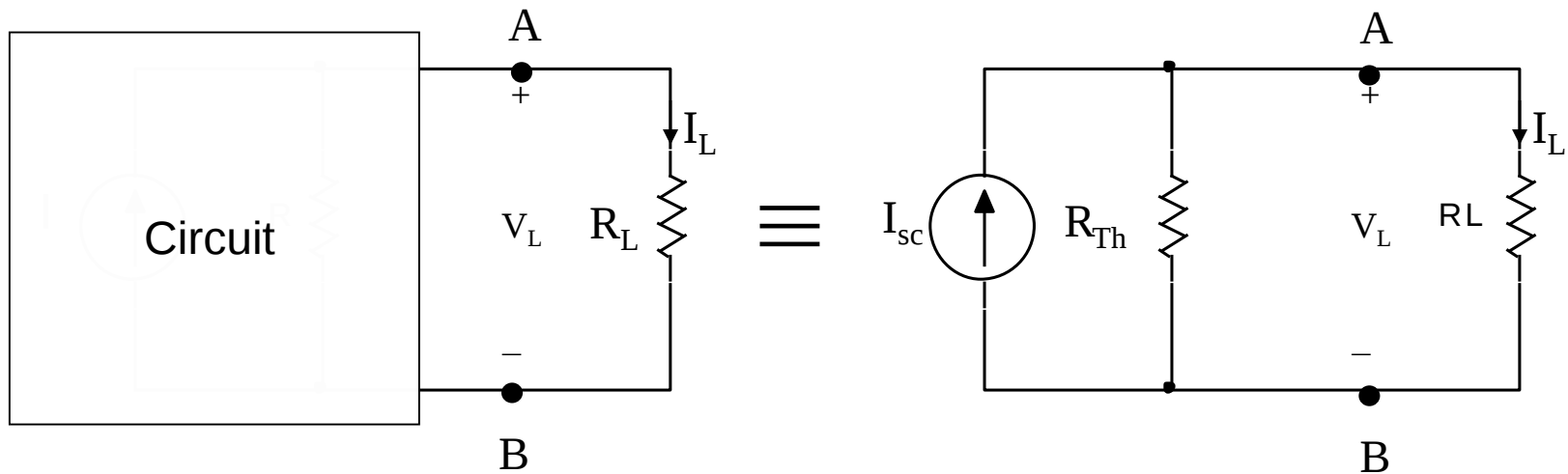

I_{sc} : Short-circuit current between terminals A & B

R_{Th} : Equivalent resistance between terminals A & B with all independent sources set to zero

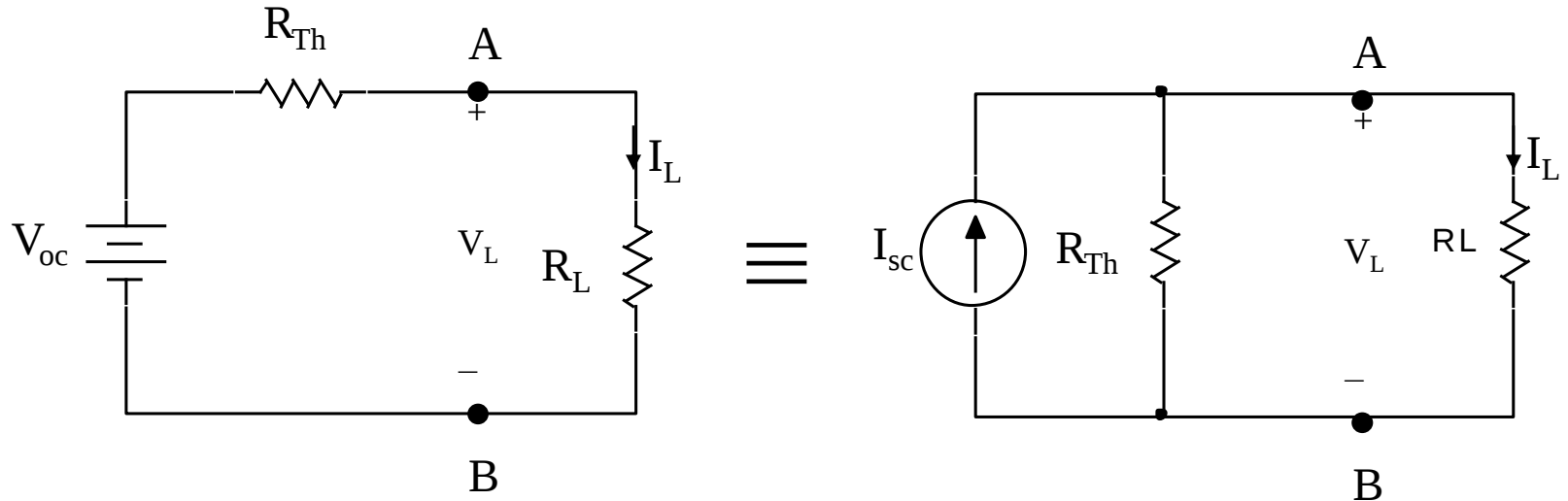Thevenin's and Norton's Equivalent Circuits



Applying source transformation theorem:


$$V_{oc}/R_{Th} = I_{sc}$$

Applying Norton's Theorem

- Replace the load by a short circuit
- Find I_{sc} by applying all known circuit analysis techniques
- Determine the equivalent resistance of the circuit at the terminals (R_{Th})
- Connect the load to I_{sc} and R_{Th} and determine the required current or voltage.

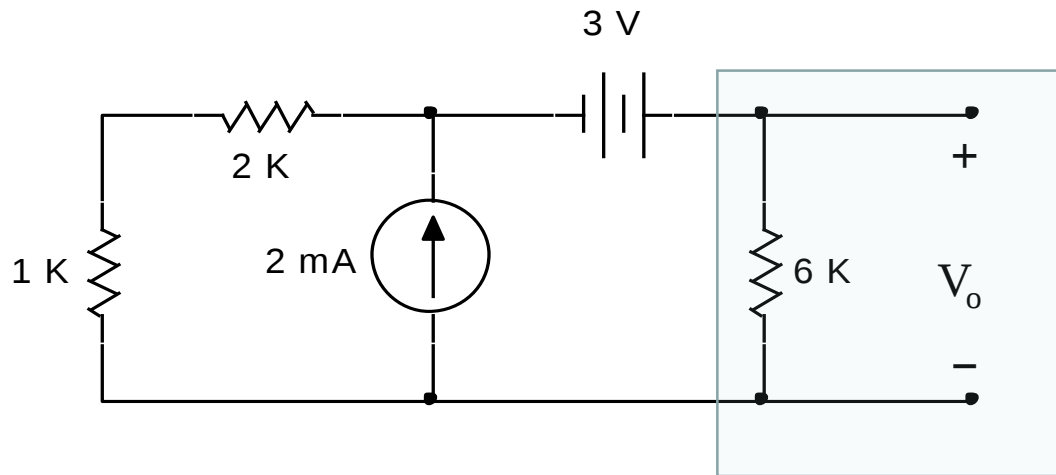Example #1


Find the voltage V_o using
(b) Norton's theorem



Solution using Norton's Theorem

1- Short-circuit the load terminals

2- Calculate I_{sc}

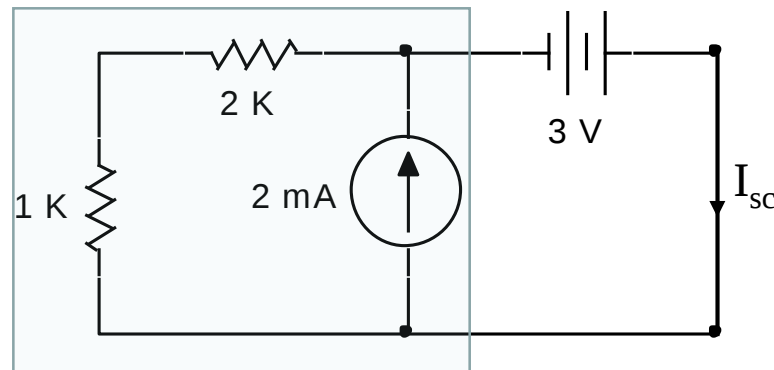


Using source transformation, we get a 6 V source in series with a resistor and the 3 V source →

$$I_{sc} = (3 + 6) / 3\text{ K} = 3\text{ mA}$$

Solution using Norton's Theorem

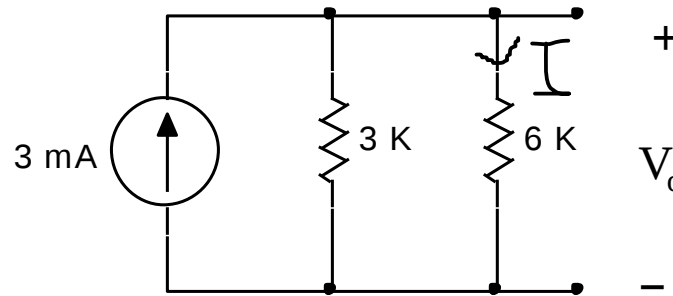- 3- R_{Th} is calculated following the same procedure of Thevenin's theorem.
- 4- Connect the load to Norton's equivalent circuit, and calculate V_o



$$V_o = 3 \text{ mA} * (6//3) = 6 \text{ V}$$


$$I = 3 \left(\frac{3}{3+6} \right)$$

$$V_o = I \times 6$$

$$V_o = 6 \times 3 \left(\frac{3}{3+6} \right)$$

Example #2

Use Norton's theorem to find I_o

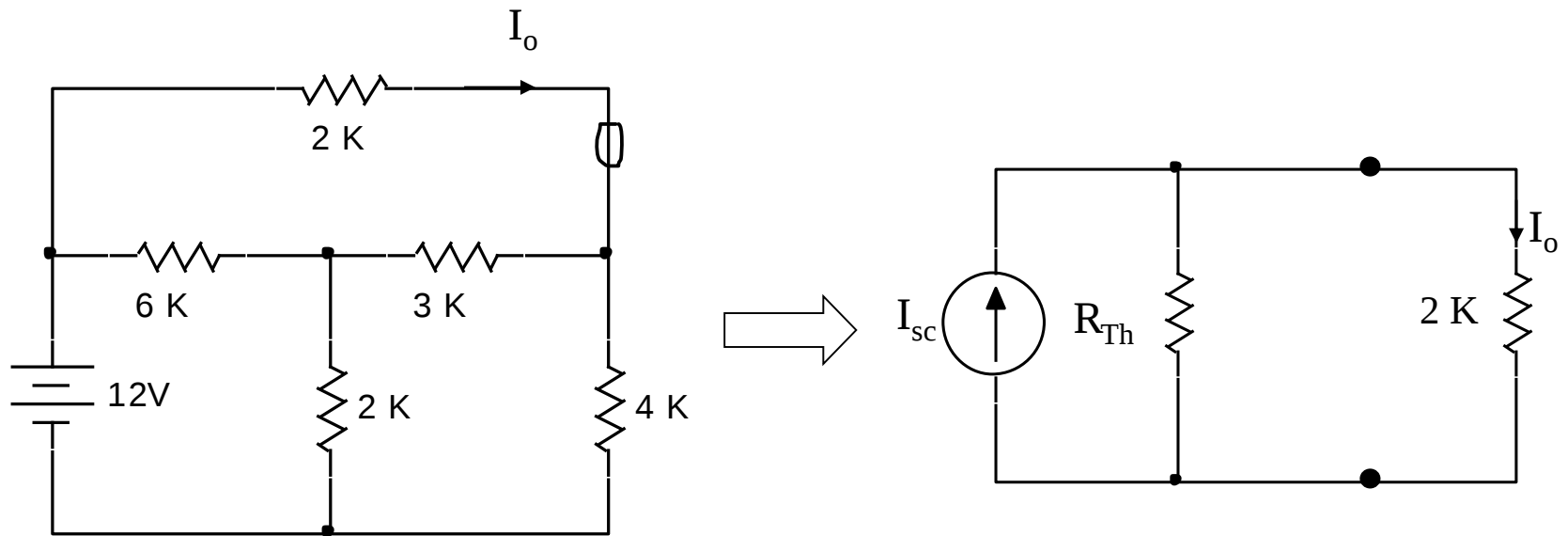

Solution

Using nodal analysis

$$V_1 = 12$$


Assuming that all currents are leaving node 2:

$$(V_2 - 12)/6 + (V_2 - 12)/3 + V_2/2 = 0$$


$$\rightarrow V_2 = 6 \text{ V}$$

Applying KCL At node 1:
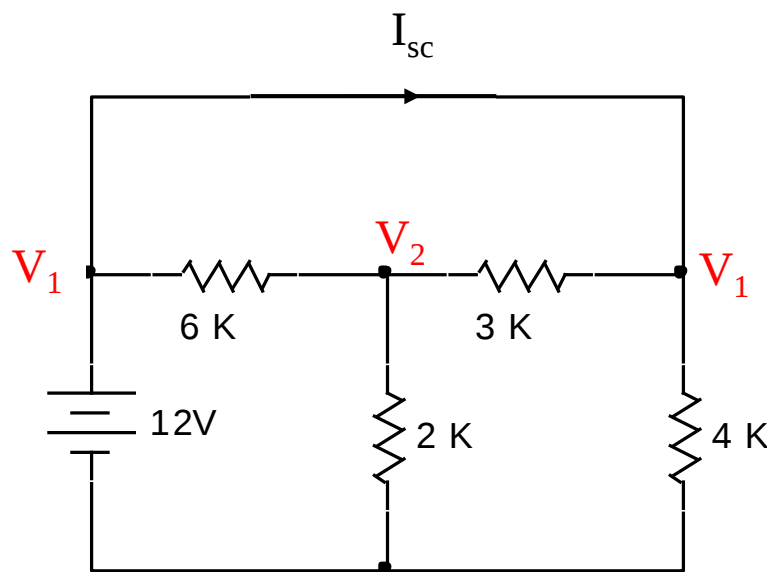
$$\begin{aligned} I_{sc} &= (12 - V_2)/3 + 12/4 \\ &= 5 \text{ mA} \end{aligned}$$




Solution

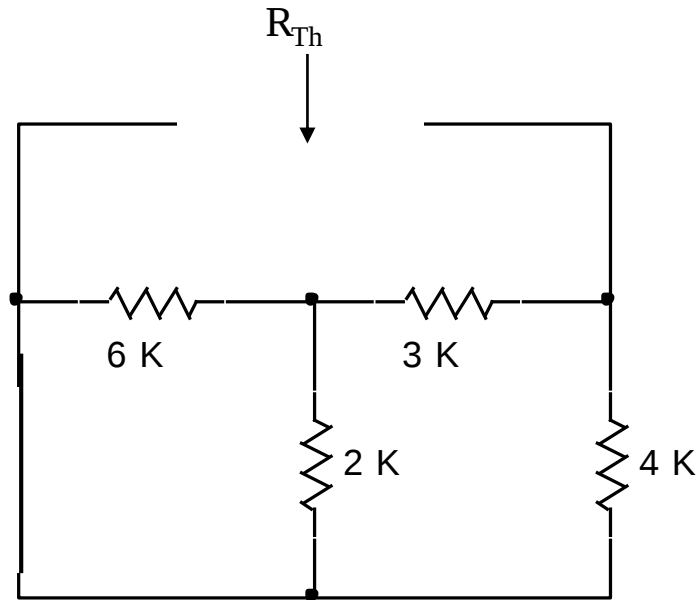

$$\begin{aligned} R_{Th} &= 4 \parallel (3 + 6 \parallel 2) \\ &= 2.12 \text{ K} \end{aligned}$$

Solution

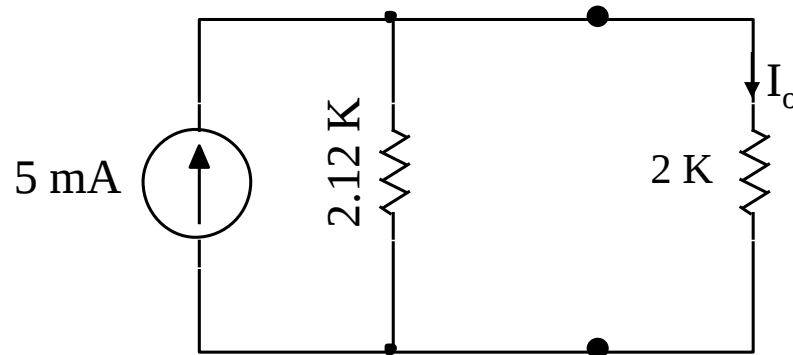

Connecting the load to Norton's equivalent circuit

$$\begin{aligned}\rightarrow I_o &= 5 * 2.12 / (2.12+2)K \\ &= 10.6 / 4.12 K = 2.57 \text{ mA}\end{aligned}$$

Exercises

Exercise#1

Example 4.8 Find the Thevenin equivalent circuit of the circuit shown in Fig. 4.27, to the left of the terminals $a - b$. then find the current through $R_L = 6, 16$, and 36Ω .

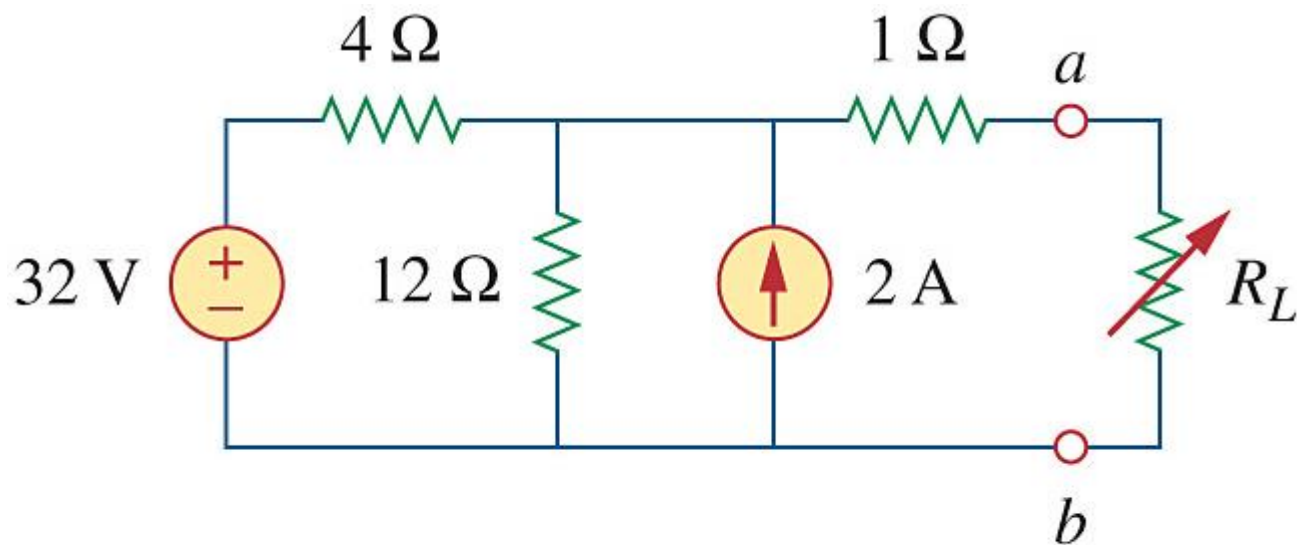


Figure 4.27

5
5**Solution :**

Turn off all independent sources, the circuit becomes what is shown in Fig. 4.28(a). Thus,

$$R_{Th} = 4 \parallel 12 + 1 = \frac{4 \times 12}{4 + 12} + 1 = 4 \text{ (W)}$$

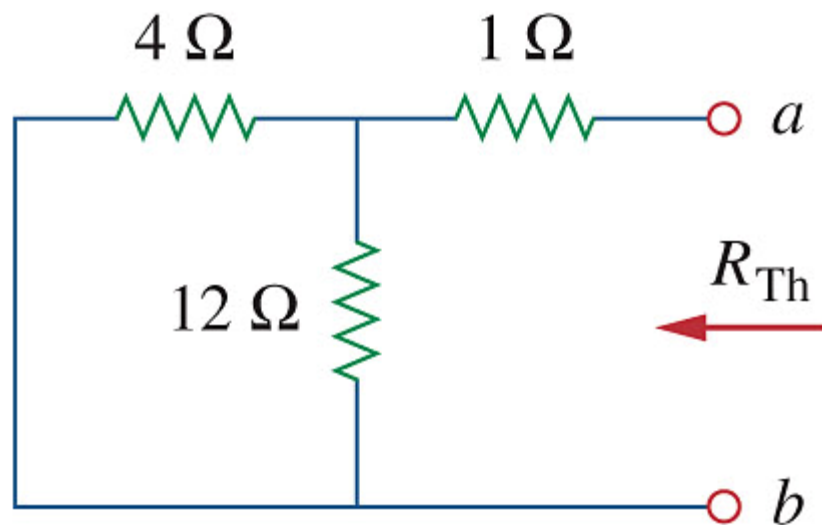


Figure 4.28(a)

5
6

Open-circuiting R_L , the circuit becomes the one in Fig. 4.28(b).

$$\frac{V_{Th} - 32}{4} + \frac{V_{Th}}{12} - 2 = 0 \Rightarrow V_{Th} = 30 \text{ (V)}$$

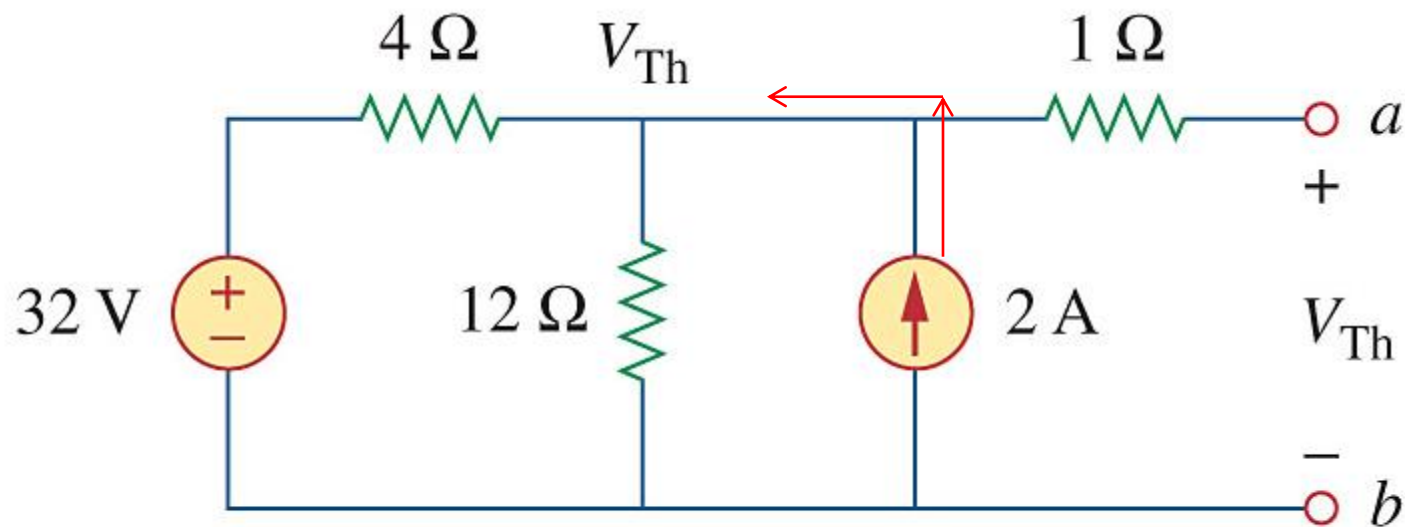


Figure 4.28(b)

The circuit in Fig. 4.27 can be replaced by the circuit shown in Fig. 4.29.

$$I_L = \frac{V_{Th}}{R_{Th} + R_L} = \frac{30}{4 + R_L} = 3, 1.5, 0.75 \text{ (A)}$$

when $R_L = 6, 16, 26 \Omega$.

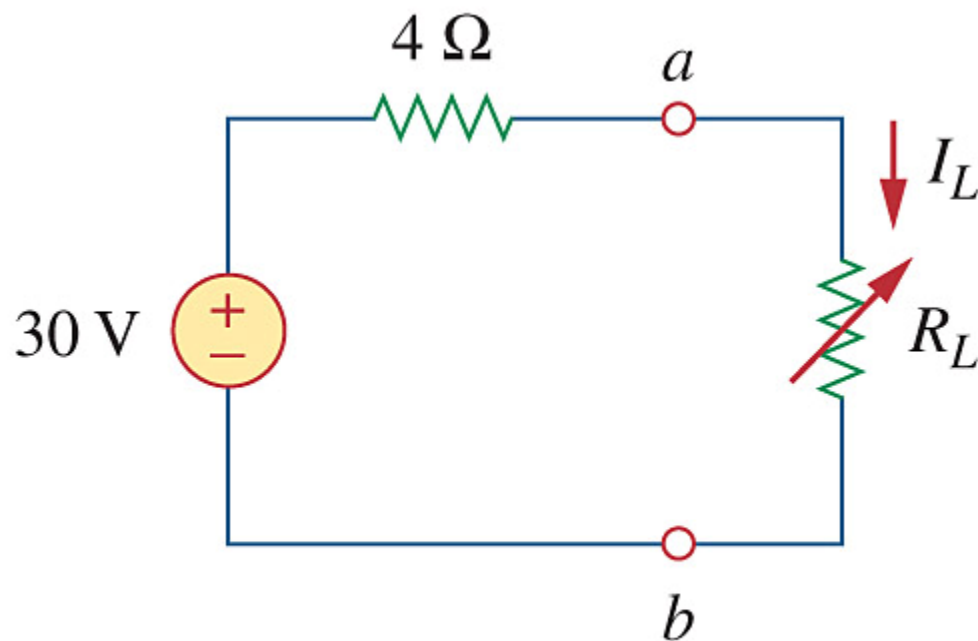


Figure 4.29

Exercise #2

Practice Problem 4.9 Find the Thevenin equivalent circuit of the circuit in Fig. 4.34 to the left of the terminals.


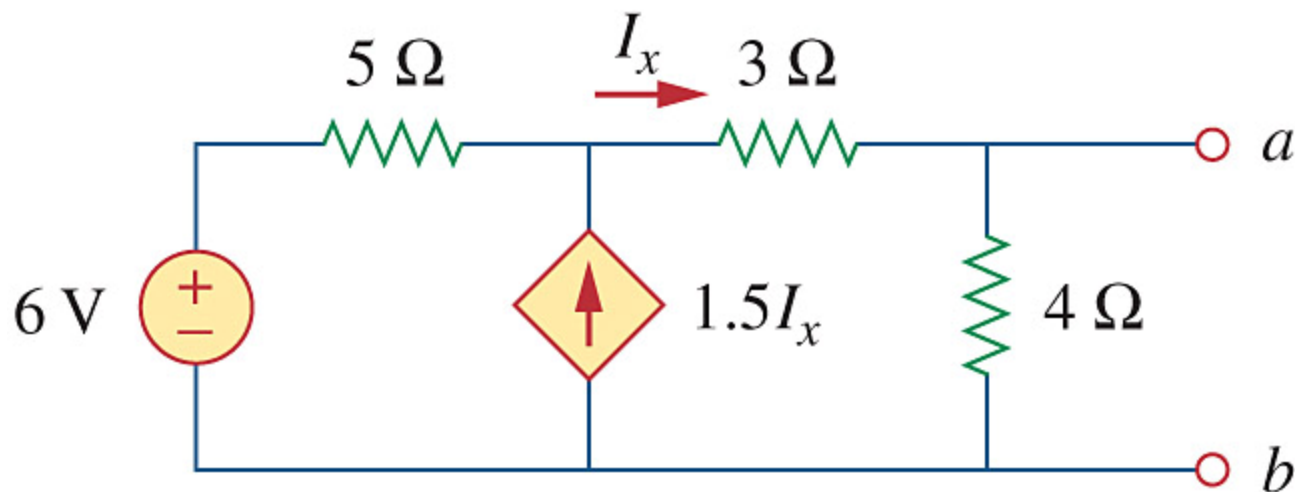


Figure 4.34

Solution :

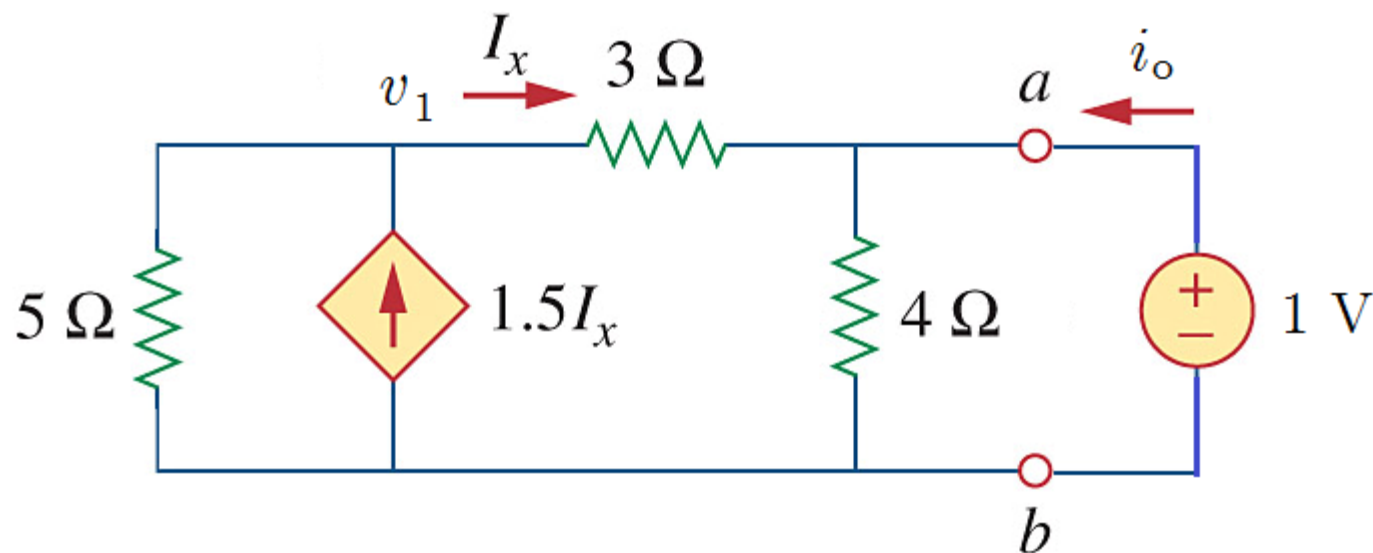To find R_{Th} , we turn off the independent voltage source and apply a test voltage source at the terminals $a - b$.



For Practice Problem 4.9: Find the Thevenin resistance


60

$$\begin{cases} I_x = \frac{v_1 - 1}{3} \\ \frac{v_1}{5} + I_x = 1.5I_x \end{cases}$$

$$\Rightarrow I_x = -2 \text{ (A)}$$

$$i_o = -I_x + \frac{1}{4} = \frac{9}{4} \text{ (A)}$$
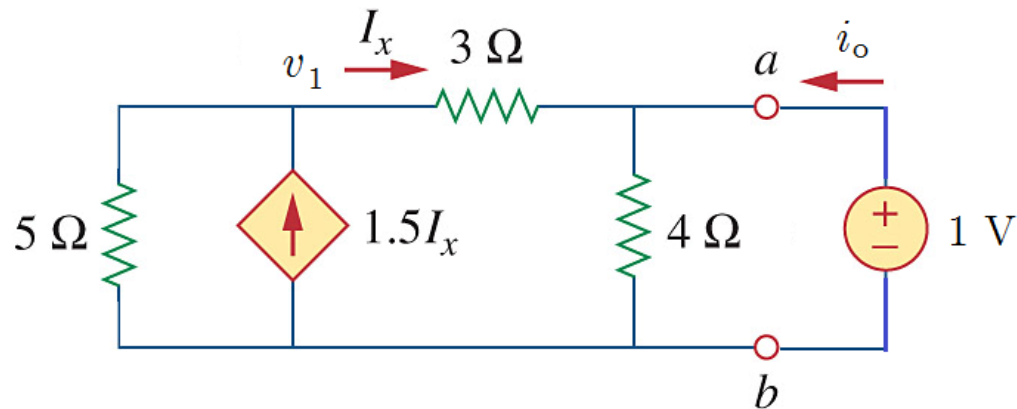
$$R_{Th} = \frac{1}{i_o} = \frac{4}{9} \approx 0.44 \text{ (}\Omega\text{)}$$



For Practice Problem 4.9: Find the Thevenin resistance

6
1


V_{Th} is the terminal voltage $V_{ab} = 4I_x$.

$$I_x = \frac{v_1}{3+4}$$


$$\Rightarrow I_x = \frac{4}{3} \text{ (A)}$$

$$\frac{6}{5} + I_x = 1.5I_x$$
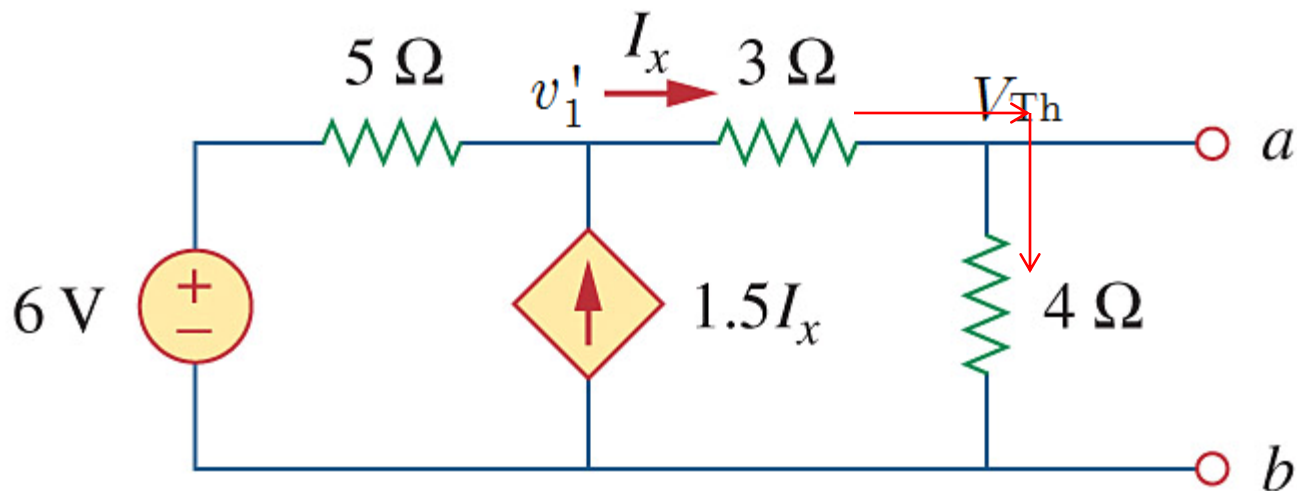
$$V_{Th} = 4I_x = \frac{16}{3} \gg 5.33 \text{ (V)}$$



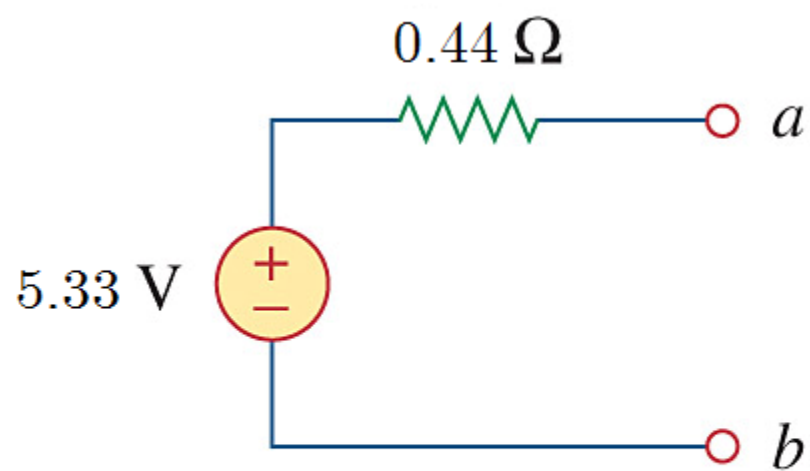For Practice Problem 4.9: Find the Thevenin voltage.



For Practice Problem 4.9:
The Thevenin Equivalent.

Exercise #3

Practice Problem 4.11 Find the Norton equivalent circuit for the circuit in Fig. 4.42, at terminals $a - b$.


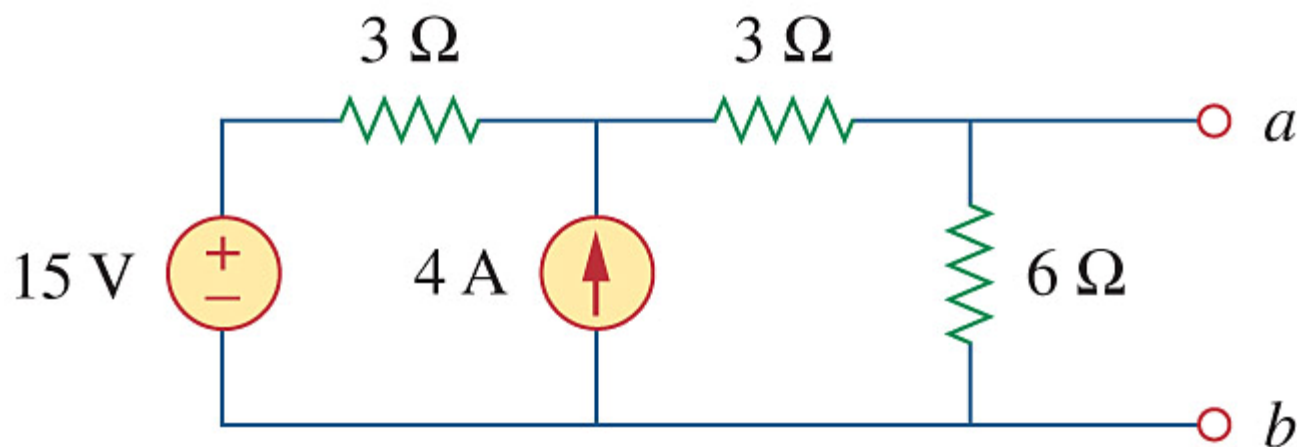


Figure 4.42

6
4**Solution :**

Turn off the voltage and current sources,
the Norton resistance is
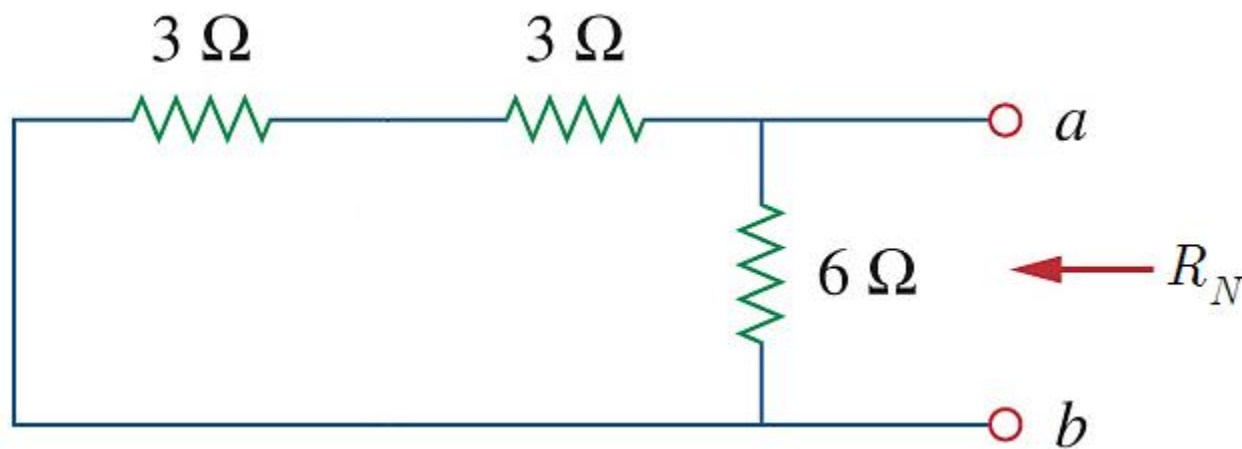
$$R_N = (3 + 3) \parallel 6 = 6 \parallel 6 = 3 \text{ } (\Omega)$$




6

5


Short-circuit terminals a and b , ignore the $6\text{-}\Omega$ resistor, apply superposition principle,
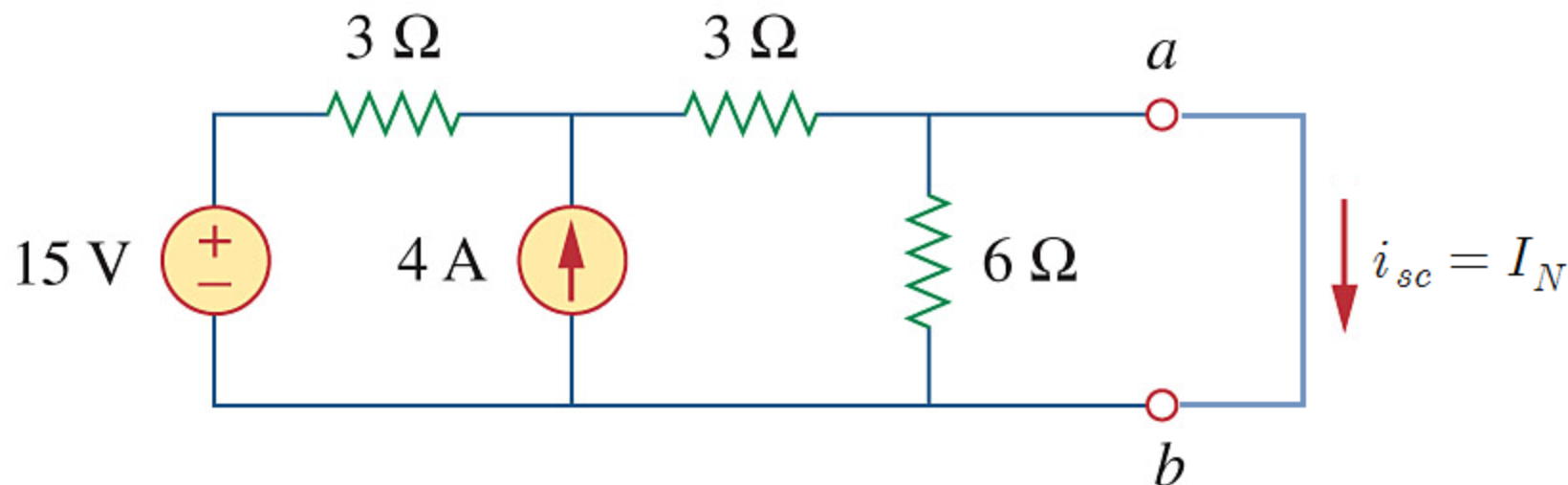
$$I_N = I'_N + I''_N = \frac{15}{3+3} + 4 \times \frac{3}{3+3} = \frac{9}{2} = 4.5 \text{ (A)}$$






6
6

The Norton equivalent is shown below.

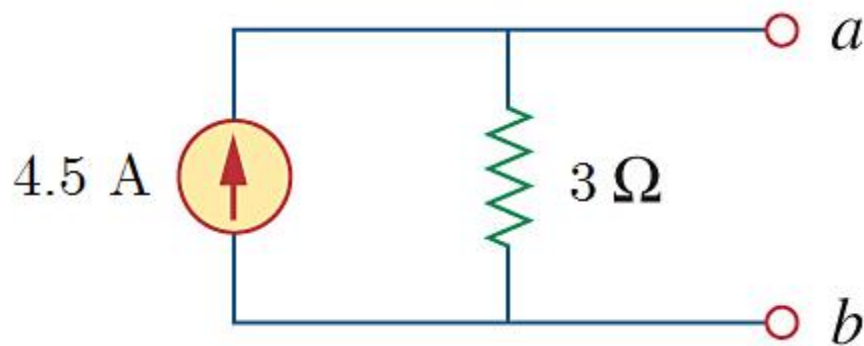

Exercise #4

Use Thevenin's theorem to find V_o

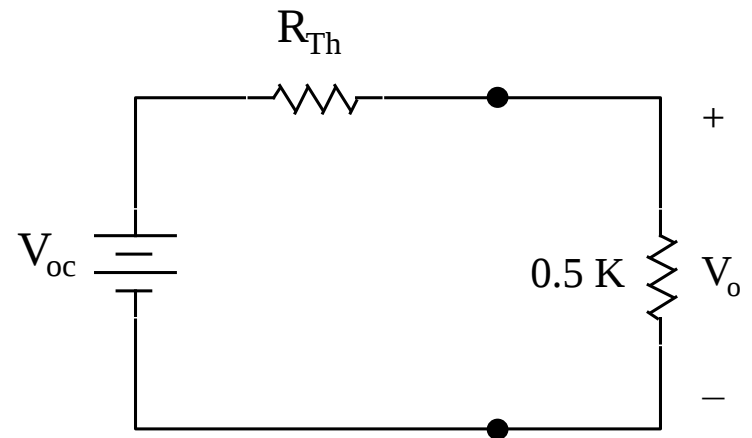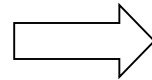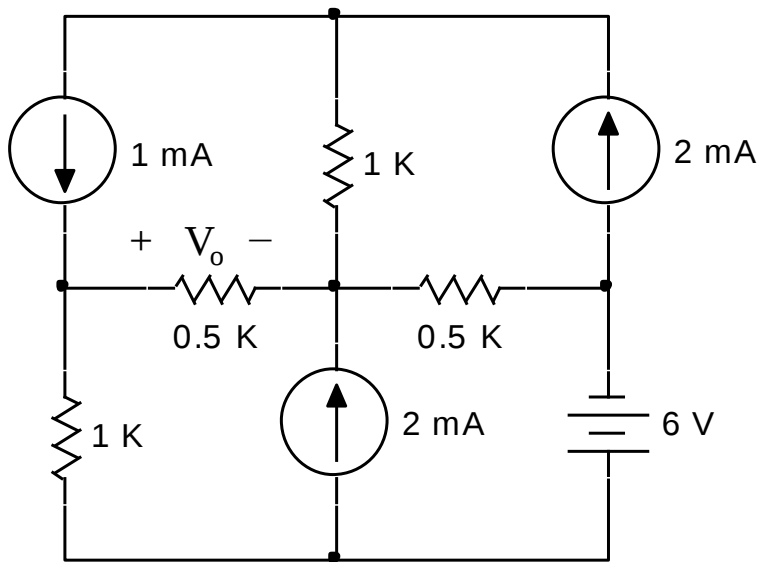

Solution

$$V_{oc} = V_1 - V_2$$

$$V_1 = 1 \text{ K} * 1 \text{ mA} = 1 \text{ V}$$

Applying KCL at node 4:


$$I_1 = 2 \text{ mA} - 1 \text{ mA} = 1 \text{ mA}$$

Applying KCL at node 2:


$$I_2 = 1 \text{ mA} + 2 \text{ mA} = 3 \text{ mA}$$

$$V_2 = 0.5 * I_2 - 6 = -4.5 \text{ V}$$
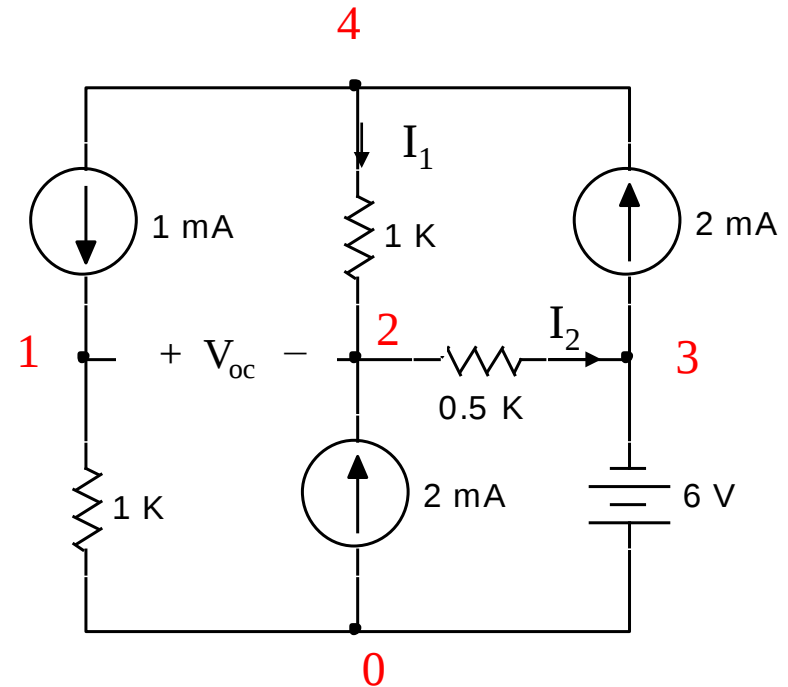
$$\begin{aligned} V_{oc} &= V_1 - V_2 \\ &= 1 - (-4.5) = 5.5 \text{ V} \end{aligned}$$




Solution

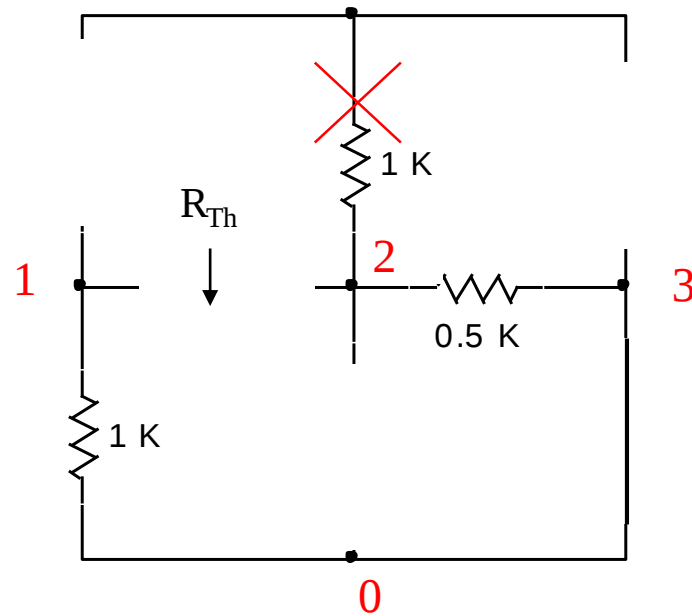

$$\begin{aligned} R_{Th} &= 1\text{ K} + 0.5\text{ K} \\ &= 1.5\text{ K} \end{aligned}$$

Solution

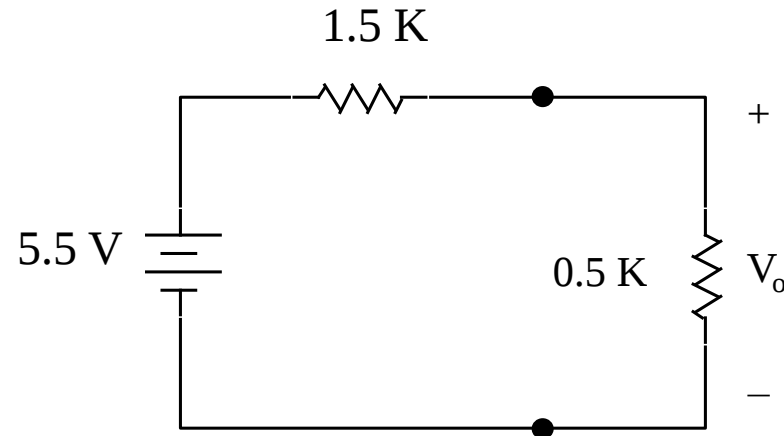

Connecting the load to Thevenin's equivalent circuit

$$\begin{aligned}\rightarrow V_o &= 5.5 * 0.5 / (1.5 + 0.5) \text{ K} \\ &= 2.75 / 2 \text{ K} = 1.375 \text{ V}\end{aligned}$$